

# **Principles of Computer Architecture**

*Miles Murdocca and Vincent Heuring*

## **Appendix B: Reduction of Digital Logic**

# Chapter Contents

**B.1 Reduction of Combinational Logic and Sequential Logic**

**B.2 Reduction of Two-Level Expressions**

**B.3 State Reduction**



# Reduction (Simplification) of Boolean Expressions

- It is usually possible to simplify the canonical SOP (or POS) forms.
- A smaller Boolean equation generally translates to a lower gate count in the target circuit.
- We cover three methods: algebraic reduction, Karnaugh map reduction, and tabular (Quine-McCluskey) reduction.

# Reduced Majority Function Circuit

- Compared with the AND-OR circuit for the unreduced majority function, the inverter for C has been eliminated, one AND gate has been eliminated, and one AND gate has only two inputs instead of three inputs. Can the function be reduced further? How do we go about it?

Unreduced

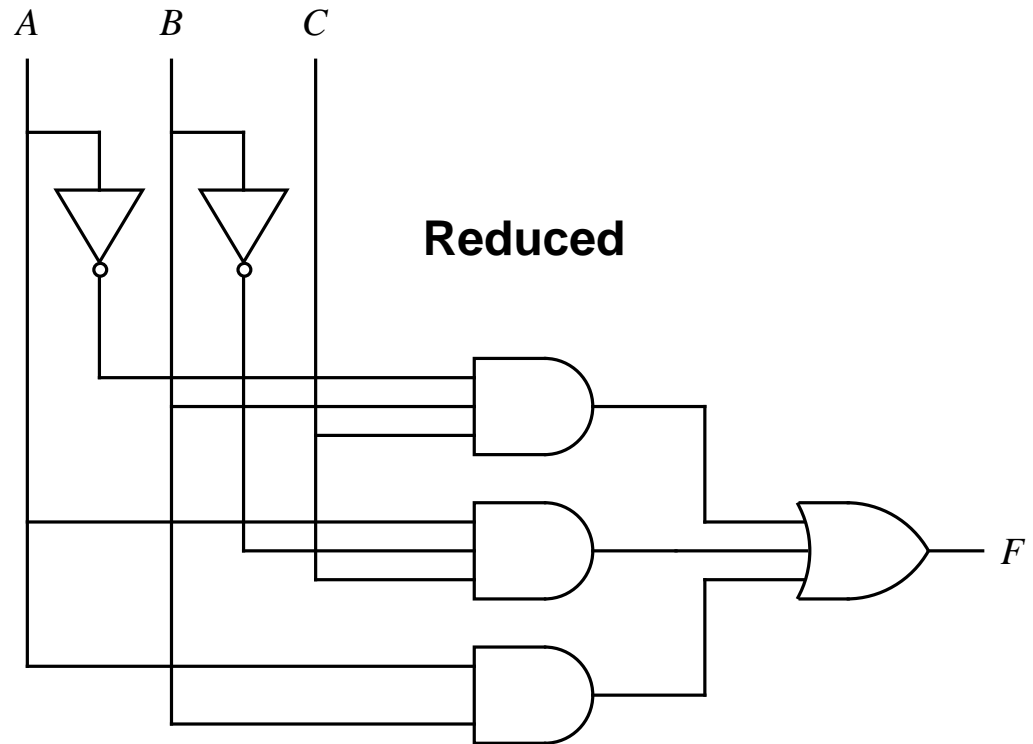 

# The Algebraic Method

- Consider the majority function,  $F$ . We apply the algebraic method to reduce  $F$  to its minimal two-level form:

$$F = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$F = \bar{A}BC + A\bar{B}C + AB(\bar{C} + C) \quad \text{Distributive Property}$$

$$F = \bar{A}BC + A\bar{B}C + AB(1) \quad \text{Complement Property}$$

$$F = \bar{A}BC + A\bar{B}C + AB \quad \text{Identity Property}$$

$$F = \bar{A}BC + A\bar{B}C + AB + ABC \quad \text{Idempotence}$$

$$F = \bar{A}BC + AC(\bar{B} + B) + AB \quad \text{Identity Property}$$

$$F = \bar{A}BC + AC + AB \quad \text{Complement and Identity}$$


$$F = \bar{A}BC + AC + AB + ABC \quad \text{Idempotence}$$

$$F = BC(\bar{A} + A) + AC + AB \quad \text{Distributive}$$

$$F = BC + AC + AB \quad \text{Complement and Identity}$$


 
# The Algebraic Method

- This majority circuit is functionally equivalent to the previous majority circuit, but this one is in its minimal two-level form:


  
# Karnaugh Maps: Venn Diagram Representation of Majority Function

- Each distinct region in the “Universe” represents a minterm.
- This diagram can be transformed into a *Karnaugh Map*.



# K-Map for Majority Function

- Place a “1” in each cell that corresponds to that minterm.
- Cells on the outer edge of the map “wrap around”

Minterm Index	A	B	C	F
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

		$AB$			
		00	01	11	10
$C$	0			1	
	1		1	1	1




# Adjacency Groupings for Majority Function

$C \backslash AB$	00	01	11	10
0			1	
1		1	1	1

- $F = BC + AC + AB$


# Minimized AND-OR Majority Circuit

 


- $F = BC + AC + AB$
- The K-map approach yields the same minimal two-level form as the algebraic approach.
 
# K-Map Groupings

- Minimal grouping is on the left, non-minimal (but logically equivalent) grouping is on the right.
- To obtain minimal grouping, create *smallest* groups first.



 
$$F = \bar{A}B\bar{C} + \bar{A}CD + ABC + A\bar{C}D$$



$$F = BD + \bar{A}B\bar{C} + \bar{A}CD + ABC + A\bar{C}D$$


# K-Map Corners are Logically Adjacent

 


$$F = B C D + \bar{B} \bar{D} + \bar{A} B$$
 
# K-Maps and Don't Cares

- There can be more than one minimal grouping, as a result of don't cares.



 
$$F = \overline{B} \overline{C} \overline{D} + B D$$



$$F = \overline{A} \overline{B} \overline{D} + B D$$
 
# Five-Variable K-Map


- Visualize two 4-variable K-maps stacked one on top of the other; groupings are made in three dimensional cubes.



$$F = \overline{A} \overline{C} D \overline{E} + \overline{A} B \overline{D} \overline{E} + B E$$
 
# Six-Variable K-Map


- Visualize four 4-variable K-maps stacked one on top of the other; groupings are made in three dimensional cubes.



$$G = \overline{B} \overline{C} \overline{E} \overline{F} + \overline{A} B \overline{D} E$$
 
# 3-Level Majority Circuit


- K-Kap Reduction results in a reduced two-level circuit (that is, AND followed by OR. Inverters are not included in the two-level count). Algebraic reduction can result in multi-level circuits with even fewer logic gates and fewer inputs to the logic gates.




 
# Map-Entered Variables


- An example of a K-map with a map-entered variable  $D$ .



$$F = BC + \overline{A}\overline{B}\overline{C}D$$
 
# Two Map-Entered Variables

- A K-map with two map-entered variables  $D$  and  $E$ .
- $F = BC + \bar{A}\bar{C}D + BE + AB\bar{C}\bar{E}$



# Truth Table with Don't Cares

- A truth table representation of a single function with don't cares.

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>
0	0	0	0	<i>d</i>
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	<i>d</i>
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	<i>d</i>

# Tabular (Quine-McCluskey) Reduction

- Tabular reduction begins by grouping minterms for which  $F$  is nonzero according to the number of 1's in each minterm. Don't cares are considered to be nonzero.
- The next step forms a consensus (the logical form of a cross product) between each pair of adjacent groups for all terms that differ in only one variable.

Initial setup

A	B	C	D	
0	0	0	0	√
0	0	0	1	√
0	0	1	1	√
0	1	0	1	√
0	1	1	0	√
1	0	1	0	√
0	1	1	1	√
1	0	1	1	√
1	1	0	1	√
1	1	1	1	√

(a)

After first reduction

A	B	C	D	
0	0	0	-	*
0	0	-	1	√
0	-	0	1	√
0	-	1	1	√
-	0	1	1	√
0	1	-	1	√
-	1	0	1	√
0	1	1	-	*
1	0	1	-	*
-	1	1	1	√
1	-	1	1	√
1	1	-	1	√

(b)

After second reduction

A	B	C	D	
0	-	-	1	*
-	-	1	1	*
-	1	-	1	*

(c)

# Table of Choice

- The prime implicants form a set that completely covers the function, although not necessarily minimally.
- A *table of choice* is used to obtain a minimal cover set.

Prime Implicants	Minterms						
	0001	0011	0101	0110	0111	1010	1101
0 0 0 _	√						
* 0 1 1 _				√	√		
* 1 0 1 _						√	
0 _ _ 1	√	√	√		√		
_ _ 1 1		√			√		
* _ 1 _ 1			√		√		√

# Reduced Table of Choice

- In a reduced table of choice, the essential prime implicants and the minterms they cover are removed, producing the *eligible set*.
- $F = \bar{A}BC + A\bar{B}C + BD + \bar{A}D$

Eligible Set	Minterms	
	0001	0011
X 000_	√	
Y 0__1	√	√
Z __11		√

Set 1      Set 2  
 000\_      0\_\_1  
 \_\_11

# Multiple Output Truth Table

- The power of tabular reduction comes into play for multiple functions, in which minterms can be shared among the functions.

Minterm	<i>A</i>	<i>B</i>	<i>C</i>	$F_0$	$F_1$	$F_2$
$m_0$	0	0	0	1	0	0
$m_1$	0	0	1	0	1	0
$m_2$	0	1	0	0	0	1
$m_3$	0	1	1	1	1	1
$m_4$	1	0	0	0	1	0
$m_5$	1	0	1	0	0	0
$m_6$	1	1	0	0	1	1
$m_7$	1	1	1	1	1	1

# Multiple Output Table of Choice

$$F_0(A,B,C) = \bar{A}\bar{B}\bar{C} + BC$$

$$F_1(A,B,C) = \bar{A}C + A\bar{C} + BC$$

$$F_2(A,B,C) = B$$

Prime Implicants	Min-terms	$F_0(A,B,C)$			$F_1(A,B,C)$					$F_2(A,B,C)$			
		$m_0$	$m_3$	$m_7$	$m_1$	$m_3$	$m_4$	$m_6$	$m_7$	$m_2$	$m_3$	$m_6$	$m_7$
$F_0$	* 0 0 0	√											
$F_1$	* 0 _ 1				√	√							
$F_1$	* 1 _ 0						√	√					
$F_2$	* _ 1 _									√	√	√	√
$F_{1,2}$	1 1 _							√	√			√	√
$F_{0,1,2}$	* _ 1 1		√	√		√			√		√		√




# Speed and Performance


- **The speed of a digital system is governed by:**
  - the propagation delay through the logic gates and
  - the propagation delay across interconnections.
- **We will look at characterizing the delay for a logic gate, and a method of reducing circuit depth using function decomposition.**

# Propagation Delay for a NOT Gate

- (From Hamacher *et. al.* 1990)

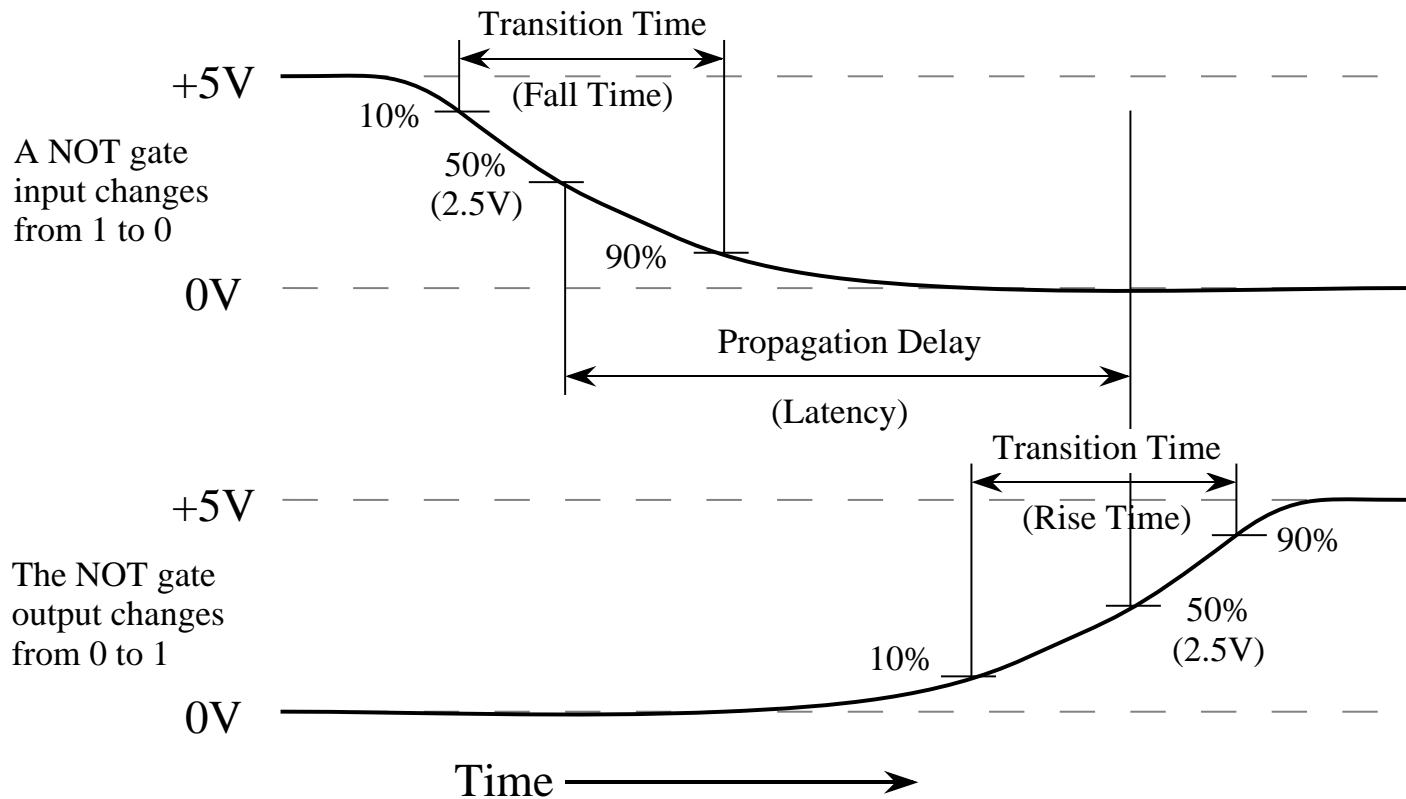



# MUX Decomposition

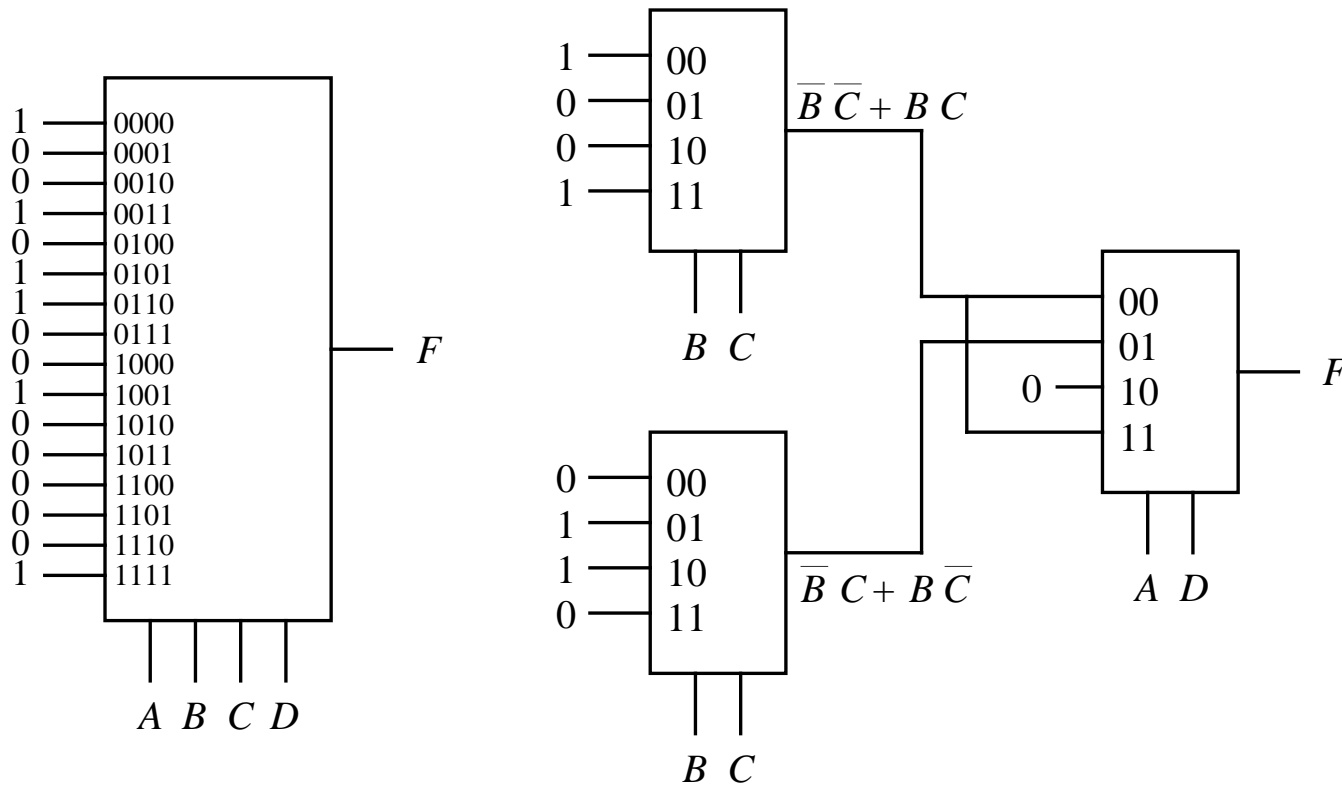

$$\begin{aligned}
 F(ABCD) &= \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}CD + \overline{A}B\overline{C}\overline{D} + \overline{A}BC\overline{D} + A\overline{B}\overline{C}\overline{D} + ABCD \\
 &= (\overline{B}\overline{C} + BC)AD + (\overline{B}C + B\overline{C})\overline{A}D + (\overline{B}\overline{C} + BC)
 \end{aligned}$$


# OR-Gate Decomposition

- Fanin affects circuit depth.

 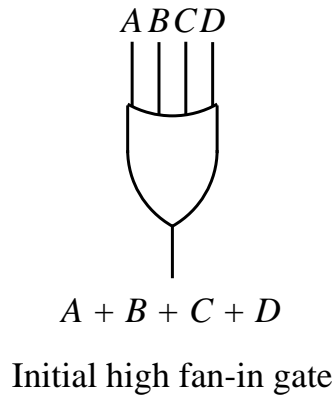

Associative law of Boolean algebra:

$$A + B + C + D = (A + B) + (C + D)$$

 

# State Reduction

- Description of state machine  $M_0$  to be reduced.

Present state \ Input	$X$	
	0	1
$A$	$C/0$	$E/1$
$B$	$D/0$	$E/1$
$C$	$C/1$	$B/0$
$D$	$C/1$	$A/0$
$E$	$A/0$	$C/1$



# Reduced State Table

- A reduced state table for machine  $M_1$ .

Current state \ Input	$X$	
	0	1
$AB: A'$	$B'/0$	$C'/1$
$CD: B'$	$B'/1$	$A'/0$
$E: C'$	$A'/0$	$B'/1$

# The State Assignment Problem

- Two state assignments for machine  $M_2$ .

P.S. \ Input	X	
	0	1
A	B/1	A/1
B	C/0	D/1
C	C/0	D/0
D	B/1	A/0

Machine  $M_2$ 

Input \ $S_0S_1$	X	
	0	1
A: 00	01/1	00/1
B: 01	10/0	11/1
C: 10	10/0	11/0
D: 11	01/1	00/0

State assignment  $SA_0$ 

Input \ $S_0S_1$	X	
	0	1
A: 00	01/1	00/1
B: 01	11/0	10/1
C: 11	11/0	10/0
D: 10	01/1	00/0

State assignment  $SA_1$



# State Assignment SA<sub>0</sub>

- Boolean equations for machine  $M_2$  using state assignment SA<sub>0</sub>.

		$X$	
		0	1
$S_0S_1$	00		
	01	1	1
	11		
	10	1	1

$$S_0 = \bar{S}_0S_1 + S_0\bar{S}_1$$

		$X$	
		0	1
$S_0S_1$	00	1	
	01		1
	11	1	
	10		1

$$S_1 = \bar{S}_0\bar{S}_1\bar{X} + \bar{S}_0S_1X + S_0S_1\bar{X} + S_0\bar{S}_1X$$

		$X$	
		0	1
$S_0S_1$	00	1	1
	01		1
	11	1	
	10		

$$Z = \bar{S}_0\bar{S}_1 + \bar{S}_0X + S_0S_1\bar{X}$$

# State Assignment SA<sub>1</sub>

- Boolean equations for machine  $M_2$  using state assignment SA<sub>1</sub>.

		X	
		0	1
S <sub>0</sub> S <sub>1</sub>	00		
	01	1	1
	11	1	1
	10		

$$S_0 = S_1$$


		X	
		0	1
S <sub>0</sub> S <sub>1</sub>	00	1	
	01	1	
	11	1	
	10	1	

$$S_1 = \bar{X}$$

		X	
		0	1
S <sub>0</sub> S <sub>1</sub>	00	1	1
	01		1
	11		
	10	1	

$$Z = \bar{S}_1\bar{X} + \bar{S}_0X$$
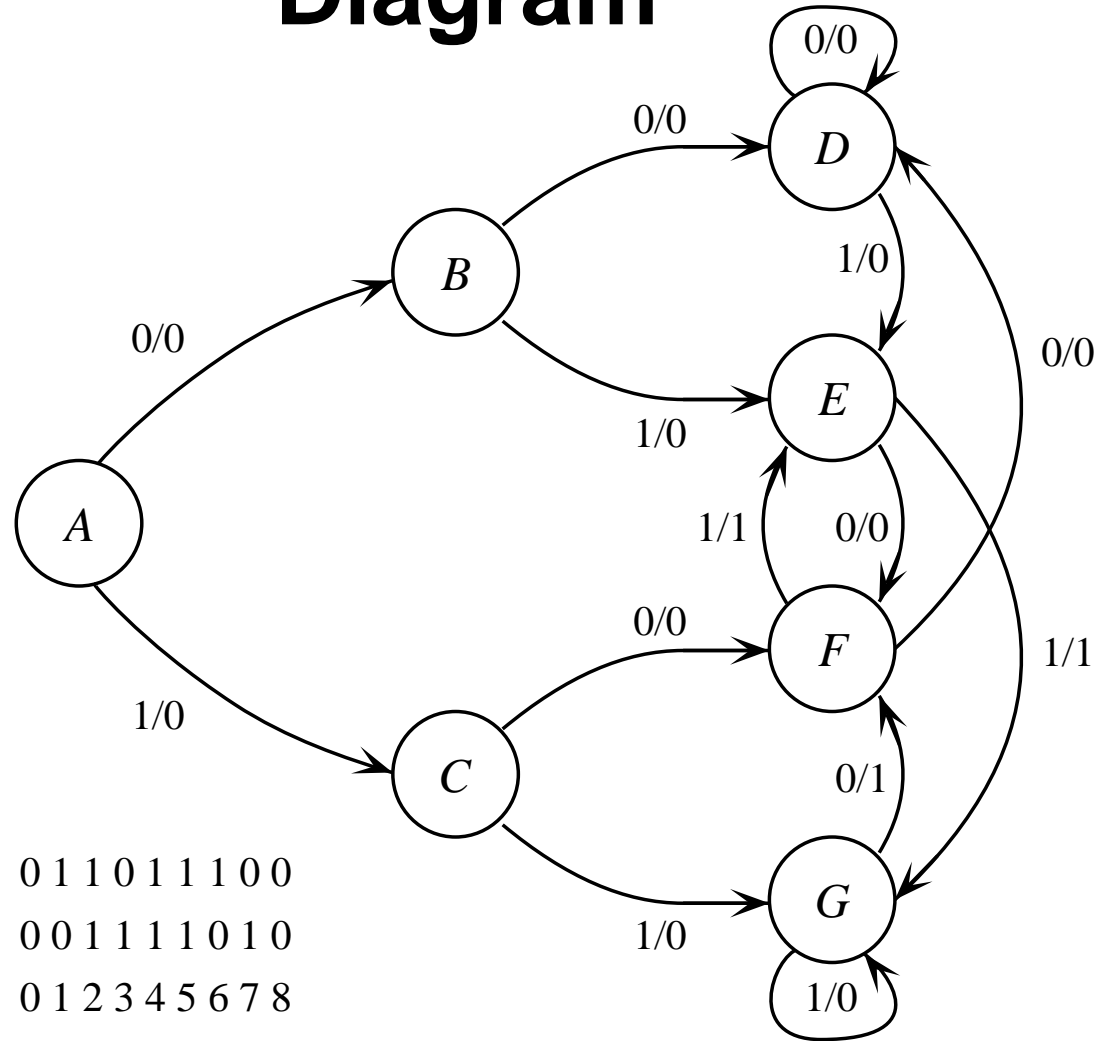
# Sequence Detector State Transition Diagram



Input: 0 1 1 0 1 1 1 0 0  
 Output: 0 0 1 1 1 1 0 1 0  
 Time: 0 1 2 3 4 5 6 7 8

# Sequence Detector State Table

Present state \ Input	<i>X</i>	
	0	1
<i>A</i>	<i>B</i> /0	<i>C</i> /0
<i>B</i>	<i>D</i> /0	<i>E</i> /0
<i>C</i>	<i>F</i> /0	<i>G</i> /0
<i>D</i>	<i>D</i> /0	<i>E</i> /0
<i>E</i>	<i>F</i> /0	<i>G</i> /1
<i>F</i>	<i>D</i> /0	<i>E</i> /1
<i>G</i>	<i>F</i> /1	<i>G</i> /0

# Sequence Detector Reduced State Table


Present state \ Input	X	
	0	1
A: A'	B'/0	C'/0
BD: B'	B'/0	D'/0
C: C'	E'/0	F'/0
E: D'	E'/0	F'/1
F: E'	B'/0	D'/1
G: F'	E'/1	F'/0

# Sequence Detector State Assignment

Present state \ Input	X	
	0	1
$S_2S_1S_0$	$S_2S_1S_0Z$	$S_2S_1S_0Z$
$A': 000$	001/0	010/0
$B': 001$	001/0	011/0
$C': 010$	100/0	101/0
$D': 011$	100/0	101/1
$E': 100$	001/0	011/1
$F': 101$	100/1	101/0
 
# Excitation Tables

- In addition to the D flip-flop, the S-R, J-K, and T flip-flops are used as delay elements in finite state machines.
- A Master-Slave J-K flip-flop is shown below.



# Sequence Detector K-Maps

- K-map reduction of next state and output functions for sequence detector.

	$S_2S_1$	00	01	11	10
$S_0X$	00	1		$d$	1
	01		1	$d$	1
	11	1	1	$d$	1
	10	1		$d$	

$$S_0 = \bar{S}_2\bar{S}_1\bar{X} + S_0X + S_2\bar{S}_0 + S_1X$$

	$S_2S_1$	00	01	11	10
$S_0X$	00			$d$	
	01	1		$d$	1
	11	1		$d$	
	10			$d$	

$$S_1 = \bar{S}_2\bar{S}_1X + S_2\bar{S}_0X$$

	$S_2S_1$	00	01	11	10
$S_0X$	00		1	$d$	
	01		1	$d$	
	11		1	$d$	1
	10		1	$d$	1

$$S_2 = S_2S_0 + S_1$$


	$S_2S_1$	00	01	11	10
$S_0X$	00			$d$	
	01			$d$	1
	11		1	$d$	
	10			$d$	1

$$Z = S_2\bar{S}_0X + S_1S_0X + S_2S_0\bar{X}$$



 
# Clocked T Flip-Flop

- Logic diagram and symbol for a T flip-flop.




Circuit

 

Symbol

# Sequence Detector Circuit

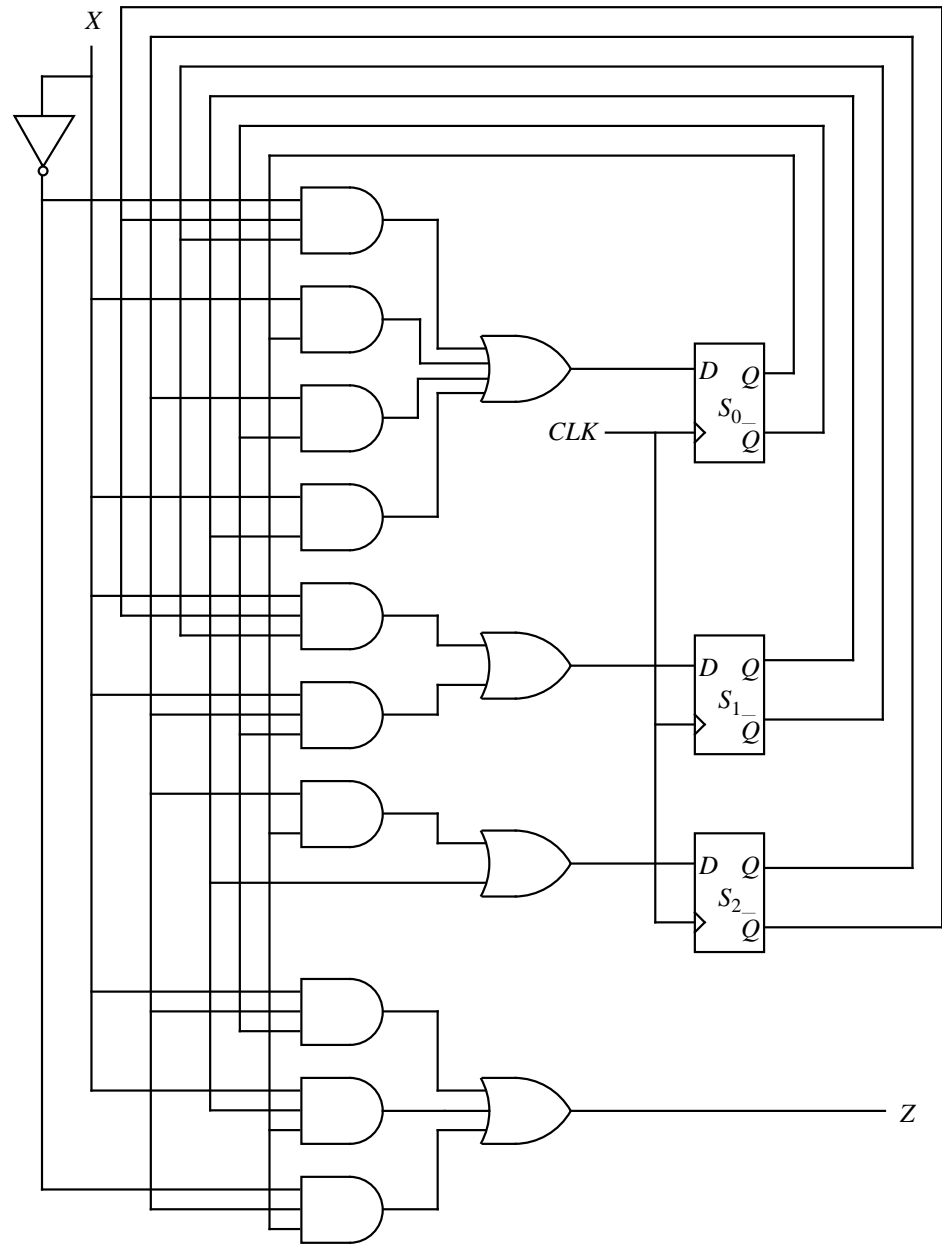

# Excitation Tables

- Each table shows the settings that must be applied at the inputs at time  $t$  in order to change the outputs at time  $t+1$ .

*S-R  
flip-flop*

$Q_t$	$Q_{t+1}$	$S$	$R$
0	0	0	0
0	1	1	0
1	0	0	1
1	1	0	0

*D  
flip-flop*

$Q_t$	$Q_{t+1}$	$D$
0	0	0
0	1	1
1	0	0
1	1	1



*J-K  
flip-flop*

$Q_t$	$Q_{t+1}$	$J$	$K$
0	0	0	$d$
0	1	1	$d$
1	0	$d$	1
1	1	$d$	0

*T  
flip-flop*

$Q_t$	$Q_{t+1}$	$T$
0	0	0
0	1	1
1	0	1
1	1	0

# Serial Adder

 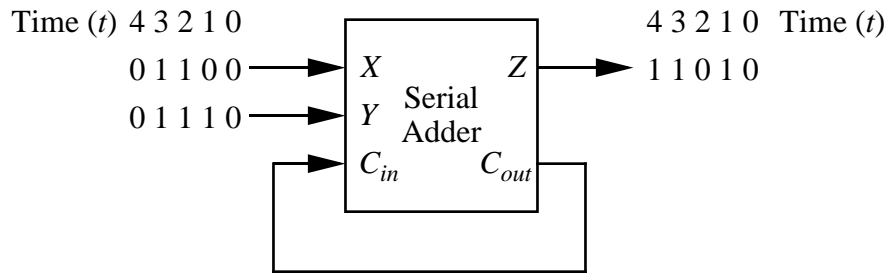

- **State transition diagram, state table, and state assignment for a serial adder.**

	Input	XY			
Present state		00	01	10	11
A		A/0	A/1	A/1	B/0
B		A/1	B/0	B/0	B/1

Next state      Output

	Input	XY			
Present state ( $S_i$ )		00	01	10	11
A:0		0/0	0/1	0/1	1/0
B:1		0/1	1/0	1/0	1/1

# Serial Adder Next-State Functions

- Truth table showing next-state functions for a serial adder for D, S-R, T, and J-K flip-flops. Shaded functions are used in the example.


Present State			(Set) (Reset)						
<i>X</i>	<i>Y</i>	<i>S<sub>t</sub></i>	<i>D</i>	<i>S</i>	<i>R</i>	<i>T</i>	<i>J</i>	<i>K</i>	<i>Z</i>
0	0	0	0	0	0	0	0	<i>d</i>	0
0	0	1	0	0	1	1	<i>d</i>	1	1
0	1	0	0	0	0	0	0	<i>d</i>	1
0	1	1	1	0	0	0	<i>d</i>	0	0
1	0	0	0	0	0	0	0	<i>d</i>	1
1	0	1	1	0	0	0	<i>d</i>	0	0
1	1	0	1	1	0	1	1	<i>d</i>	0
1	1	1	1	0	0	0	<i>d</i>	0	1

# J-K Flip-Flop Serial Adder Circuit


$$J = XY$$

$$K = \bar{X}\bar{Y}$$

 
$$Z = \bar{X}\bar{Y}S + \bar{X}Y\bar{S} + XY\bar{S} + X\bar{Y}S$$



# D Flip-Flop Serial Adder Circuit

 

# Majority Finite State Machine

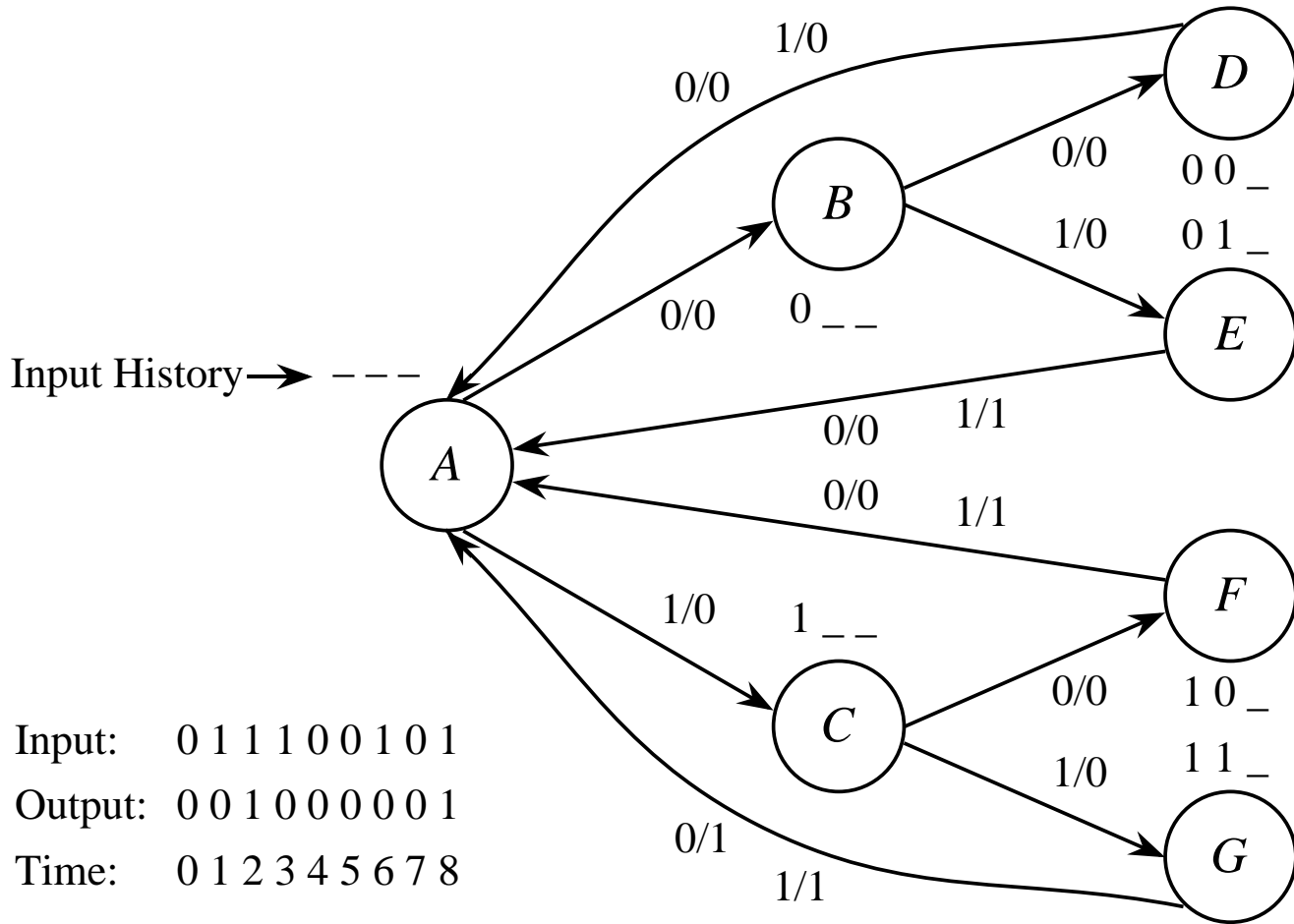



# Majority FSM State Table

- (a) State table for majority FSM; (b) partitioning; (c) reduced state table.

P.S. \ Input	X	
	0	1
A	B/0	C/0
B	D/0	E/0
C	F/0	G/0
D	A/0	A/0
E	A/0	A/1
F	A/0	A/1
G	A/1	A/1

(a)

$$\begin{aligned}
 P_0 &= (ABCDEFGG) \\
 P_1 &= (ABCD)(EF)(G) \\
 P_2 &= (AD)(B)(C)(EF)(G) \\
 P_3 &= (A)(B)(C)(D)(EF)(G) \\
 P_4 &= (A)(B)(C)(D)(EF)(G) \checkmark
 \end{aligned}$$

(b)

P.S. \ Input	X	
	0	1
A: A'	B'/0	C'/0
B: B'	D'/0	E'/0
C: C'	E'/0	F'/0
D: D'	A'/0	A'/0
EF: E'	A'/0	A'/1
G: F'	A'/1	A'/1

(c)

# Majority FSM State Assignment

- (a) State assignment for reduced majority FSM using D flip-flops; and (b) using T flip-flops.

Input		X	
		0	1
P.S.			
	$S_2S_1S_0$	$S_2S_1S_0Z$	$S_2S_1S_0Z$
$A'$ :	000	001/0	010/0
$B'$ :	001	011/0	100/0
$C'$ :	010	100/0	101/0
$D'$ :	011	000/0	000/0
$E'$ :	100	000/0	000/1
$F'$ :	101	000/1	000/1

(a)

Input		X	
		0	1
P.S.			
	$S_2S_1S_0$	$T_2T_1T_0Z$	$T_2T_1T_0Z$
$A'$ :	000	001/0	010/0
$B'$ :	001	000/0	010/0
$C'$ :	010	110/0	111/0
$D'$ :	011	011/0	011/0
$E'$ :	100	100/0	100/1
$F'$ :	101	101/1	101/1

(b)

# Majority FSM Circuit

